 


Logic Design Spring 2021 Midterm Exam II


Name:

Student ID Number:

1. For each of the following statements, answer if it is true or false.
 - a. "And" gate is functionally complete. (2 points)
 - b. In Verilog, the symbols "~" and "!" are functionally different for one bit operand. (2 points)
 - c. In Verilog, when declaring module outputs, they can only be "reg" type. (2 points)
 - d. In Verilog, when declaring module inputs, they can be either "reg" type or "wire" type. (2 points)
 - e. Both combinational and sequential circuits contain memory elements and logic gates. (2 points)
2. Convert 2's complement binary number 11101111 to a decimal number. (5 points)
3.
 - a. Using a decoder and OR gates only to construct a combinational circuit that implements the following two Boolean functions. (5 points)
$$F1 = yz + x'y + y'z'$$
$$F2 = (x' + y)z + xy'z$$
 - b. Redo 3(a) using a decoder and NAND gates only. (3 points)
4. Assume the delays of "not", "nand", "nor", "and", "or" and "xor" gates are 1, 2, 2, 3, 3 and 4 units, respectively.
 - a. Given the following 2-bit adder, compute the delays of outputs Q1 and C0. (5 points)



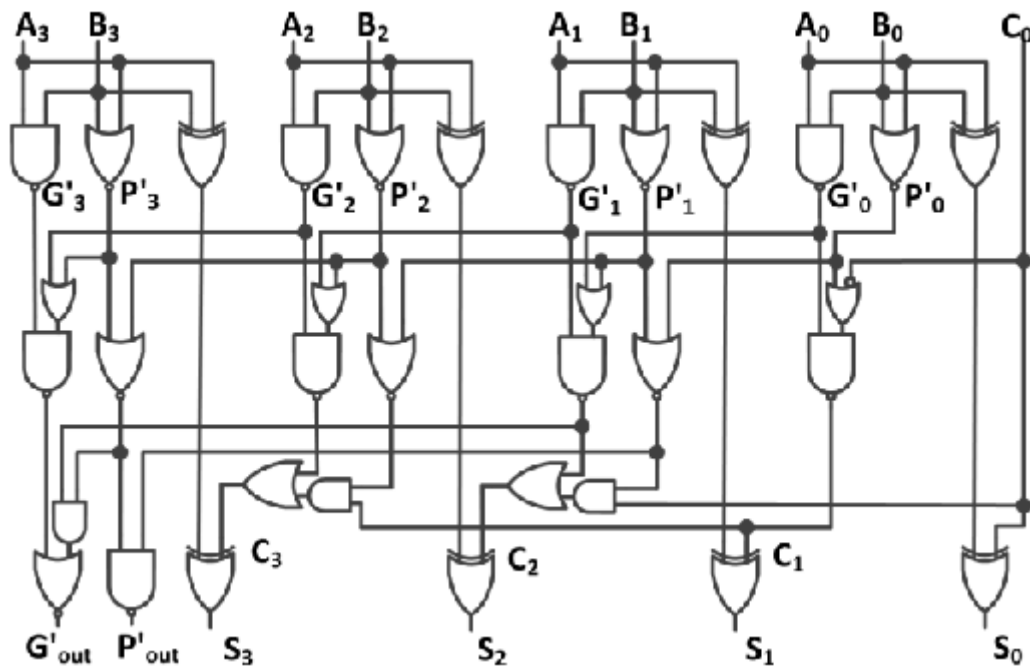- b. Given the following 4-bit carry lookahead adder, compute the delays of outputs S_3 , G'_{out} and P'_{out} . (5 points)



5.

- a. Design a combinational circuit with input $X[2 : 0]$ and outputs A , and $Y[1 : 0]$. When $(X \bmod 3)$ equals zero, A is one and Y is don't care. Otherwise, A is zero and Y is the integer part of $X / 3$. (10 points)
- b. Finish the Verilog code of the above circuit. (5 points)

```
module NTHU(X, A, Y);
    input [2:0] X;
    output A;
    output [1:0] Y;


    assign A = ?
    assign Y[1] = ?
    assign Y[0] = ?

endmodule
```

6. Given a four-input function $f(w, x, y, z) = \sum m(0, 2, 4, 5, 7, 8, 10, 11, 15) + \sum d(3, 13)$. Please answer the following questions for the function f .
- List all prime implicants. (5 points)
 - List all essential prime implicants. (5 points)

7. Construct a 5-to-32-line decoder with four 3-to-8-line decoders with enable and a 2-to-4-line decoder. Use block diagrams for the components. (5 points)

 8. Given a 4-to-1 multiplexer below.
What is the function $Y = f(A, B, C)$ it implements? (5 points)




9. Implement a full adder in two different ways below.

- Using two 8-to-1 MUXes. Connect X, Y, and C_{in} to the control inputs of the MUXes and connect 1 or 0 to each data input. (5 points)
- Using two 4-to-1 MUXes and one inverter. Connect X and Y to the control inputs of the MUXes, and connect 1, 0, C_{in} or C_{in}' to each data input. (5 points)

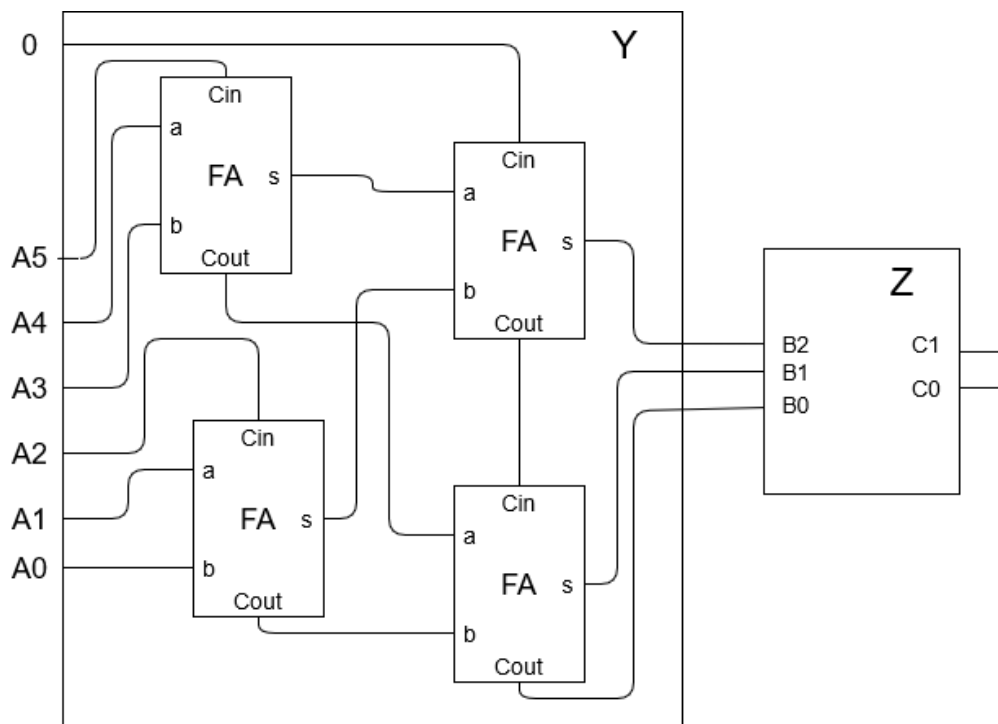
10. The circuit below contains two sub-circuits, a sub-circuit Y with input A[5: 0] and output B[2: 0], and a sub-circuit Z with input B[2: 0] and output C[1: 0].

- The “FA” components inside Y are one-bit full adders. What is the function of Y? (5 points)
- Design the combinational circuit Z, when the input B is larger than 3, the output is 2'b01, when it is smaller than 3, output is 2'b00, and when the input equals 3, C[1] is 1 and C[0] is don't care. (5 points)



11. A combinational circuit N is divided into two subcircuits N_1 and N_2 as shown. The truth table for N_1 is given.

 - a. Find the output Z as a function of A , B and C . (6 points)



- b. Assume that the input combinations $ABC=110$ and $ABC=010$ never occur. Change as many of the values of D , E and F to don't care as you can without changing the value of the output Z . (6 points)

A	B	C	D	E	F
0	0	0	1	1	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	1	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	0	1	0
1	1	1	0	0	0